



Remarks: No. of pages: 2 No. of questions: 7 Allowed Tables and Charts: (None)

Answer the following Questions (assume any required data)

Question (1)

(20Marks)

Marks

(a)	Sketch the V-I curve of silicon diode and discuss the equivalent circuit of diode in ideal, practical and complete operation cases.	[8]
(b)	Sketch the output voltage of each circuit shown in fig	[12]

Question (2)

(20Marks)

Marks

(a)	Sketch the output voltage of the voltage divider shown in fig.	[5]
	Referring to fig. sketch the rectifier output voltage the load terminal voltage, load current, diode 3 current and V_{AK} of diode 2 (without capacitor) if the transformer output is 36 v (r.m.s). assume practical diode model.	[10]
(c)	Discuss the principle of operation of half wave and full wave voltage doubler	[5]

Question (3)

(20Marks)

Marks


[a]	Explain how to connect the seven segment display (common anode) to display number (5) where the maximum continuous forward current for each LED is 30 ma and a +5 volt dc source is to be used	[8]
[b]	A loaded Zener regulator is shown in fig. 6, $V_Z = 5.1$ v, at $I_Z = 49$ ma, $I_{ZK} = 1$ ma, $Z_Z = 7 \Omega$ and $I_{Zm} = 70$ ma. Determine the minimum and maximum possible load.	[12]

Question (4) (15Marks)

Marks

For the gain transistor circuit in fig., Draw the DC equivalent circuit, then calculate:

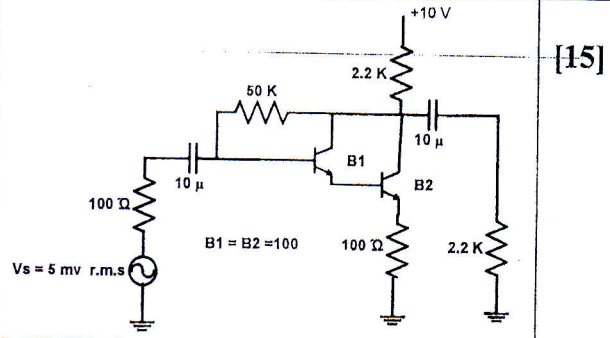- [a]
- 1-DC transistor currents I_B , I_C and I_E .
 - 2- DC transistor voltages V_E , V_B and V_C
 - 3- Collector saturation current $I_{C Sat}$
 - 4- Collector –Emitter Cut off voltage
 - 5- Centered operating point parameters




[15]

Question (5) (15Marks)

Marks

The figure shows a small-signal amplifier, drive the mathematical expression for medium frequency:

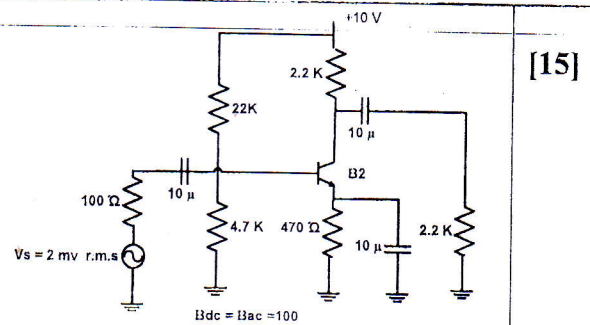- [a]
- 1- Voltage gain, current gain "overall".
 - 2- Input and output impedances.
 - 3- Calculate A_v , A_i , Z_{in} and Z_o
 - 4- Calculate the center frequency between medium and high frequency " f_2 " $C_{Jout} = 10$ nF
 - 5- Calculate the amplifier constant.




[15]

Question (6) (18Marks)

Marks

For the given multistage amplifier:

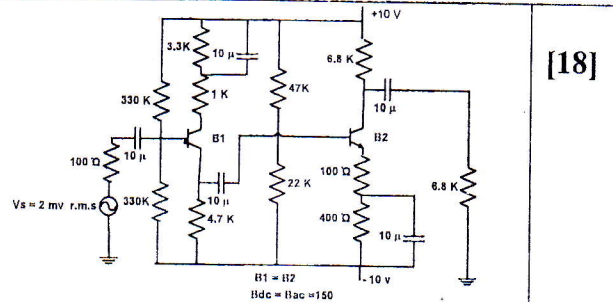- [a]
- Draw the complete AC equivalent circuit.
 - Draw the medium frequency equivalent circuit.
 - Calculate $A_{V mid}$, Z_{in} , and $Z_o mid$




[18]

Question (7) (12Marks)

Marks

Figure shows a push-pull large signal amplifier with Darlington transistor. Explain its function of operation, then :

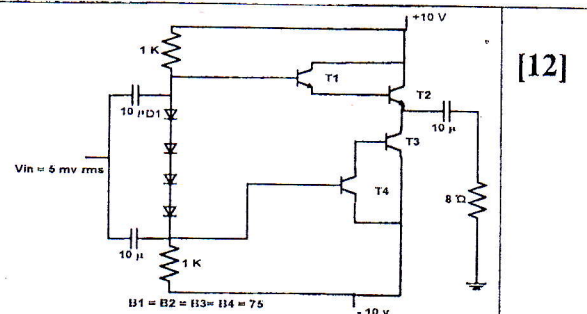- [a]
- Calculate the amplifier input DC power
 - Calculate the amplifier output AC power
 - Calculate the amplifier efficiency.



[12]

National Academic Reference Standard(NARS)

Field	National Academic Reference Standard(NARS)								
	Knowledge & Understanding				Intellectual Skills	Professional Skills			General Skills
Course ILOs	a-4-1	a-8-1	a-8-2	a-19-1	b-2-1	c-13-1	c-13-2	c-17-1	-----
Question No.	1(a), 3(b), 7	1(b), 3(a), 5(a),	1(b), 2(a,b), 4(a,b),	2(a), 3(a),	3(a), 6	1(b), 2(a), 5(b),	3(b), 5(a),	2(a), 3(a), 4(b), 7	-----

انتهت الأسئلة مع أطيب الأمنيات بالتوفيق

أ.د / عوض السيد المع

أ.د / احمد ابو مارة